
Aim: Design a LED using push button.

Apparatus: Arduino, LED's, Resistance 220,

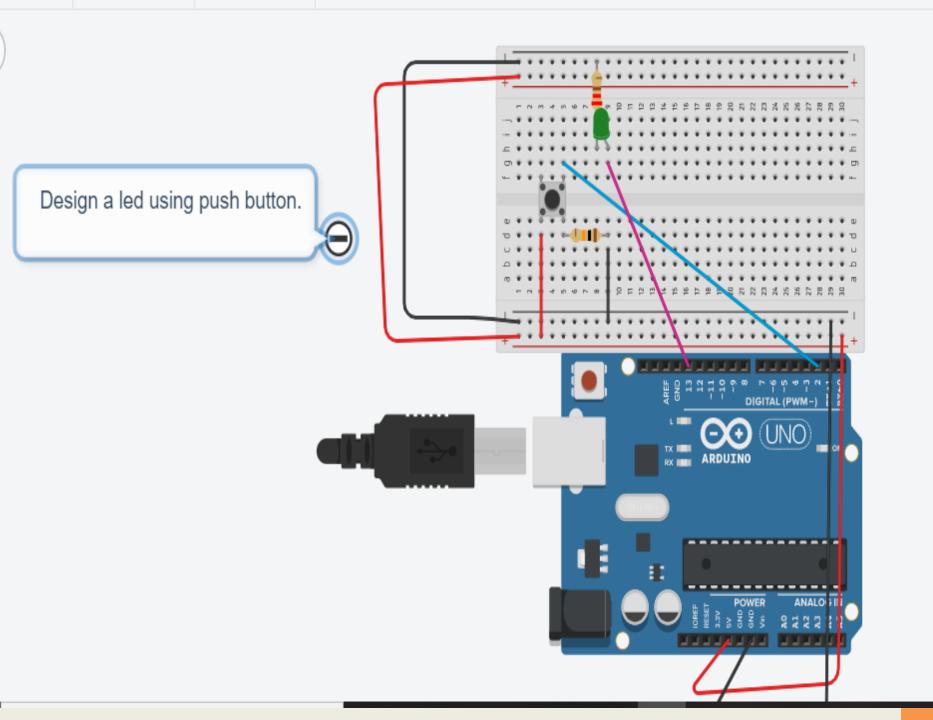10000 ohm, wires, Breadboard, Push Button



```
int buttonState = 0;
void setup()
 pinMode(2,INPUT);
 pinMode(13, OUTPUT);
void loop()
 buttonState = digitalRead(2);
 if (buttonState == HIGH) {
  digitalWrite(13, HIGH);
 else
  digitalWrite(13, LOW);
```

